



Uncontrolled Half wave

1. The half-wave rectifier circuit of Fig. 3-1a has $V_s(t) = 170 \sin(377t)$ V and a load resistance $R = 15 \Omega$. Determine (a) the average load current, (b) the rms load current, (c) the power absorbed by the load, (d) the apparent power supplied by the source, and (e) the power factor of the circuit.

2. A half-wave rectifier has a source of 120 V rms at 60 Hz and an RL load with $R = 10 \Omega$ and $L = 15 \text{ mH}$. Determine (a) an expression for load current, (b) the average current, (c) the power absorbed by the resistor, and (d) the power factor.

$$(\beta = 3.65 \text{ rad}, I_{\text{avg}} = 5.05 \text{ A}, I_{\text{rms}} = 7.64 \text{ A}, P = 585 \text{ W}, \text{PF} = 0.64)$$

3. A half-wave rectifier of Fig. 3-5a has a 240 V rms, 60 Hz ac source. The load is a series inductance, resistance, and dc source, with $L = 75 \text{ mH}$, $R = 10 \Omega$, and $V_{\text{dc}} = 100 \text{ V}$. Determine (a) an expression for load current, (b) the power absorbed by the dc voltage source, (c) the power absorbed by the resistance, and (d) power supplied by the source and the power factor.

$$(\alpha = 0.299, \beta = 3.941 \text{ rad}, P_{\text{dc}} = 313.4 \text{ W}, P_R = 231 \text{ W}, P = 544.4 \text{ W}, \text{PF} = 0.47)$$

4. A half-wave rectifier of Fig. 3-6 has a 120 V rms, 60 Hz ac source. The load is a series inductance and dc voltage with $L = 100 \text{ mH}$ and $V_{\text{dc}} = 48 \text{ V}$. Determine (a) an expression for load current, (b) Determine the power absorbed by the dc voltage source. (c) the power factor.

$$(\alpha = 0.286, \beta = 4.485 \text{ rad}, P_{\text{dc}} = 96.5 \text{ W}, \text{PF} = 0.279)$$

5. The half-wave rectifier with a freewheeling diode (Fig. 3-7a) has $R = 2 \Omega$ and $L = 25 \text{ mH}$, V_m is 100 V, and the frequency is 60 Hz. (a) Determine the average load voltage and current, and (b) the power absorbed by the resistor.

$$(V_{\text{avg}} = 31.8 \text{ V}, I_{\text{avg}} = 15.9 \text{ A}, I_{\text{rms}} = 16.34 \text{ A}, P_R = 534 \text{ W})$$

6. For the half-wave rectifier with a freewheeling diode and RL load as shown in Fig. 3-7a, the source is 240 V rms at 60 Hz and $R = 8 \Omega$. (a) Assume L is infinitely large. Determine the power absorbed by the load and the power factor as seen by the source. Sketch V_o , $iD1$, and $iD2$. (b) Determine the average current in each diode. (c) For a finite inductance, determine L such that the peak-to-peak current is no more than 10 percent of the average current.

$$(I_{\text{avg}} = 13.5 \text{ A} \approx I_{\text{rms}}, P = P_R = 1459 \text{ W}, \text{PF} = 0.637, I_{D_{\text{avg}}} = 6.75 \text{ A}, L = 0.67 \text{ H})$$

7. The half-wave rectifier of Fig. 3-11a has a 120 V rms source at 60 Hz, $R = 500 \Omega$, and $C = 100 \mu\text{F}$. Determine (a) an expression for output voltage, (b) the peak-to-peak voltage variation on the output, (c) an expression for capacitor current, (d) the peak diode current, and (e) the value of C such that ΔV_o is 1 percent of V_m .

$$(\Delta V_o = 43 \text{ V}, I_{D_{\text{peak}}} = 4.5 \text{ A}, C = 3333 \mu\text{F})$$