

Q1: Find i_L (in micro amperes) in the circuit in Fig.1

Q2: The op-amp in the circuit in Fig.2 is ideal. Calculate the following: v_1 , v_o , i_2 and i_o

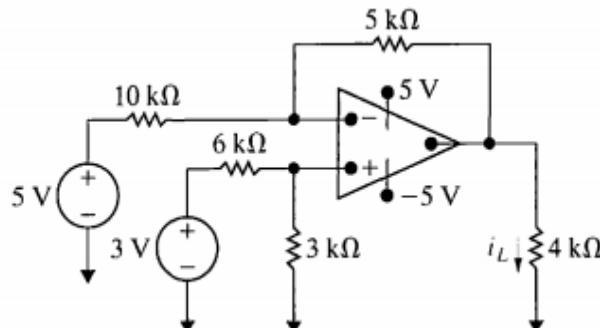


Fig.1

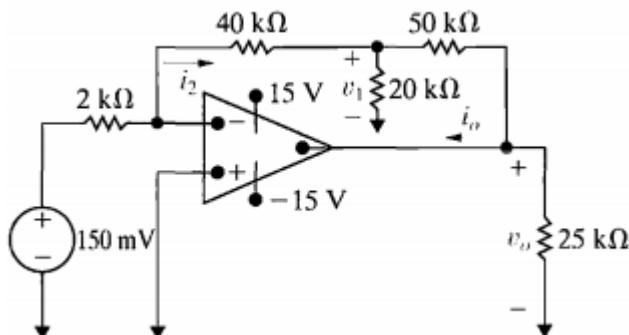


Fig.2

Q3: The op-amp in Fig.3 is ideal.

A) What circuit configuration is shown in this figure?

B) Find v_o if $v_a=1\text{ V}$, $v_b=1.5\text{ V}$ and $v_c=-4\text{ V}$.

c) The voltages v_a and v_c remain at 1 V and -4 V ,

Respectively. What are the limits on v_b if the op-amp operates within its linear region?

Q4: The op-amp in Fig.4 is ideal.

A) Calculate v_o when v_g equals 4 V .

b) Specify the range of values of v_g so that the op-amp operate in linear region.

c) Assume that v_g equals 2 V and that the 63k Resistor replaced with variable what is its value to saturate the op-amp?

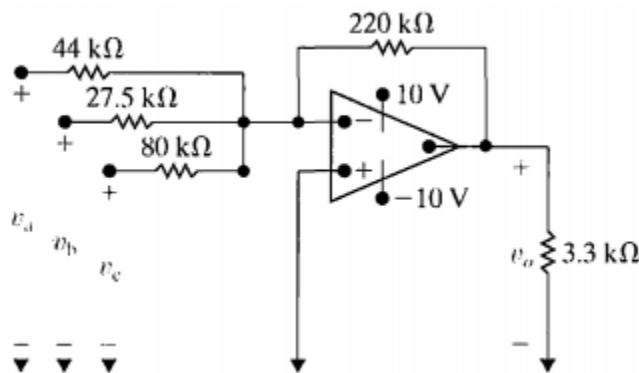


Fig.3

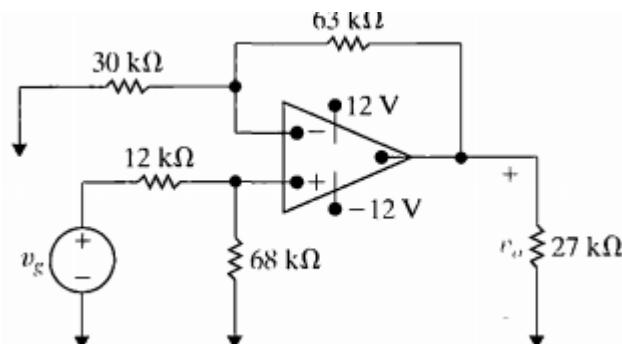


Fig.4

Q5: The circuit in Fig.5 is an non inverting summing amplifier. Assume the op-amp is ideal. Design the Circuit so that $V_o = V_a + 2V_b + 3V_c$ a) Specify the numerical values of R_a and R_c . b) Calculate i_a , i_b , and i_c (in micro amperes) when $v_a=0.7\text{ V}$, $v_b=0.4\text{ V}$, and $v_c=1.1\text{ V}$.

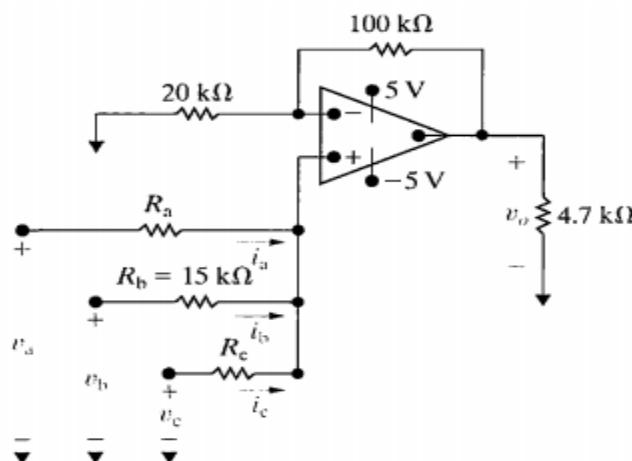


Fig.5

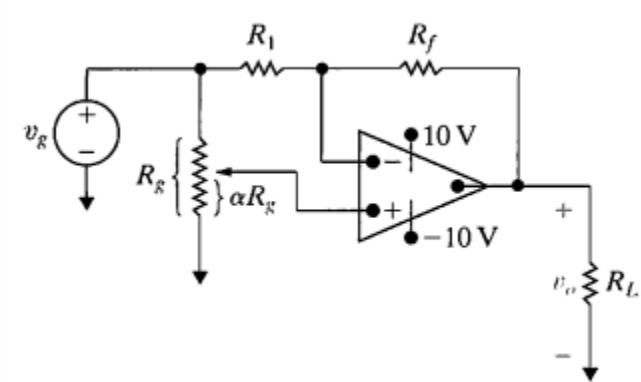



Fig.6

Q6: The op-amp in the circuit of Fig.6 is ideal.


- Plot v_o versus α when $R_f=4R_1$ and $v_g= 2V$. Use increments of 0.1 and note by hypothesis that $0<\alpha<1.0$.
- Write an equation for the straight line you plotted in(a). How are the slope and intercept of the line related to v_g and the ratio R_f/R_1 ?
- Using the results from(b), choose values for v_g and the ratio R_f/R_1 such that $v_o=-6 \alpha+4$.

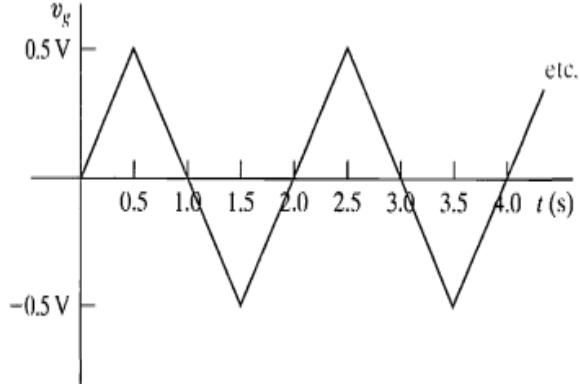Q7 : The voltage v_g shown in Fig.7 (a) is applied to the Inverting amplifier shown in Fig.7 (b).

Sketch v_o versus t , assuming the op-amp is ideal.



(a)

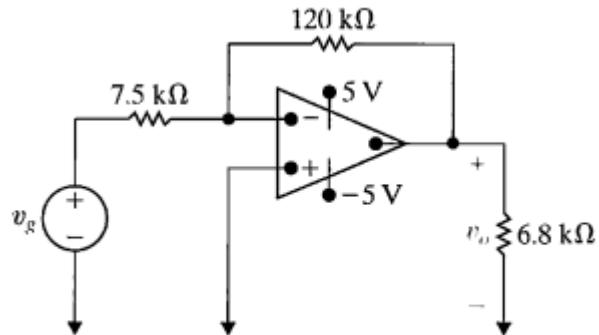

(b)

Fig.7

Q8: The op-amps in the circuit in Fig.8 are ideal .

- Find i_a .
- Find the value of the left source voltage for which $i_a=0$.

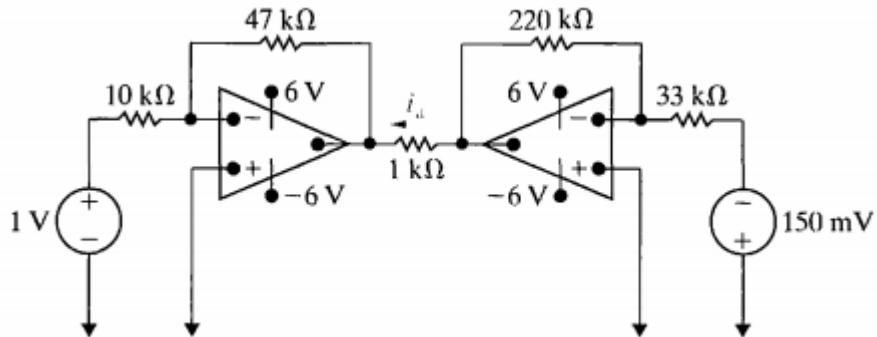


Fig.8

Q9: A four-bit R-2R ladder DAC is presented in Fig. 9

- Show that the output voltage is given by

$$-V_o = R_f \left(\frac{V_1}{2R} + \frac{V_2}{4R} + \frac{V_3}{8R} + \frac{V_4}{16R} \right)$$

- If $R_f=12 \text{ k}\Omega$ and $R=10 \text{ k}\Omega$, find $|V_o|$ for $[V_1V_2V_3V_4] = [1011]$ and $[V_1V_2V_3V_4] = [0101]$.

