
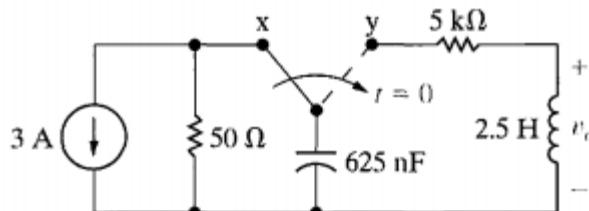


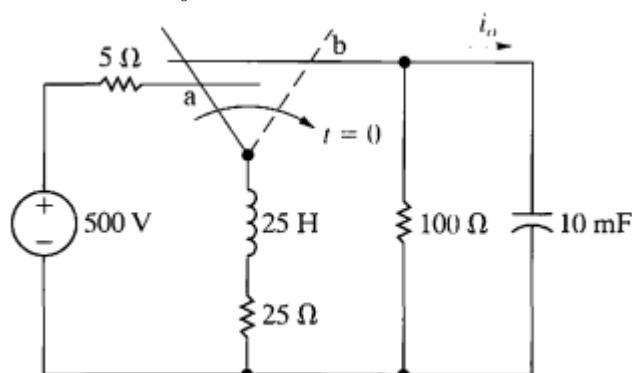**Q1)** The switch in the circuit shown in Fig.P1 has been in position x for a long time. At  $t=0$ , the switch moves instantaneously to position y.

- Construct an S-domain circuit for  $t>0$ .
- Find  $V_0$
- Find  $v_0$ .




**Q2)** The make-before-break switch in the circuit in Fig.P2 has been in position a for a long time. At  $t=0$ , it moves instantaneously to position b. Find  $i_0$  for  $t>0$ .



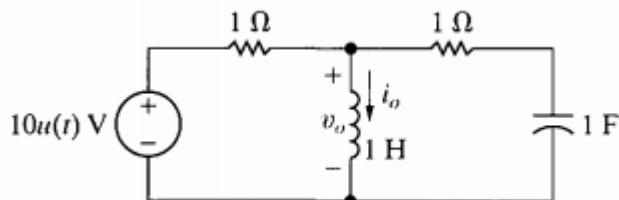
**Q3)** There is no energy stored in the circuit in Fig.P3 at  $t=0^-$

- Use the mesh current method to find  $i_0$ .
- Find the time domain expression for  $v_0$ .
- Do your answers in (a) and (b) make sense in terms of known circuit behavior? Explain.




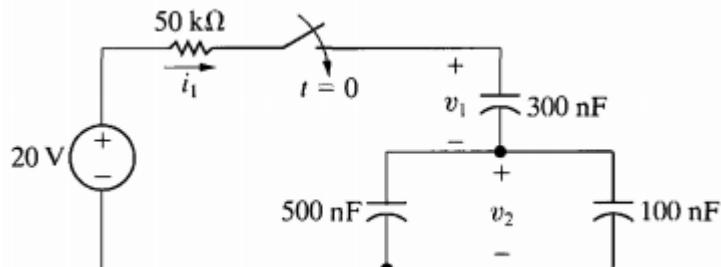**Q4)** There is no energy stored in the capacitors in the Circuit in Fig.P4 at the time the switch is closed.


- Construct the s-domain circuit for  $t>0$ .
- Find  $I_1, V_1$  and  $V_2$ .
- Find  $i_1, v_i$ , and  $v_2$ .
- Do your answers for  $i_1, v_i$ , and  $v_2$  make sense in terms of known circuit behavior? Explain.



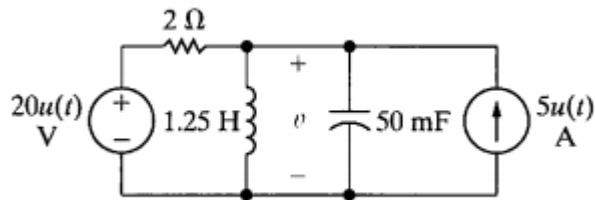**Q5)** The energy stored in the circuit shown is zero at the instant the two sources are turned on. Using superposition principle in S-domain **Find the expression for  $v$  when  $t > 0$ .**




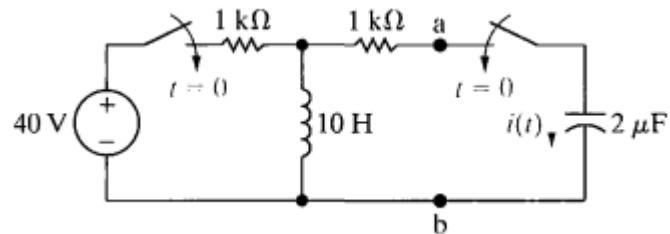**Q6)** The two switches in the circuit shown in Fig.P6 Operate simultaneously. There is no energy stored in the circuit at the instant the switches close. Find  $i(t)$  for  $t \geq 0^+$  By first finding the s-domain Thevenin equivalent of the circuit to the left of the Terminals a,b



**Q7)** The op-amp in the circuit shown in Fig.P7 is ideal. There is no energy stored in the capacitors at Instant the circuit is energized.

- Find  $v_0$  if  $v_{g1}=40u(t)$  V and  $v_{g2}=16u(t)$  V.
- How many milliseconds after the two voltage sources are turned on does the op-amp saturate?

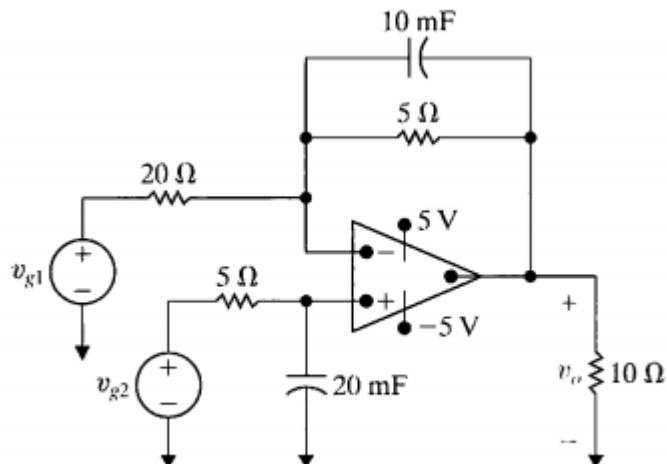

**TABLE 12.1 An Abbreviated List of Laplace Transform Pairs**

Type	$f(t)$ ( $t > 0^-$ )	$F(s)$
(impulse)	$\delta(t)$	1
(step)	$u(t)$	$\frac{1}{s}$
(ramp)	$t$	$\frac{1}{s^2}$
(exponential)	$e^{-at}$	$\frac{1}{s + a}$
(sinc)	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
(cosine)	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
(damped ramp)	$te^{-at}$	$\frac{1}{(s + a)^2}$
(damped sine)	$e^{-at} \sin \omega t$	$\frac{\omega}{(s + a)^2 + \omega^2}$
(damped cosine)	$e^{-at} \cos \omega t$	$\frac{s + a}{(s + a)^2 + \omega^2}$

**TABLE 12.2 An Abbreviated List of Operational Transforms**

Operation	$f(t)$	$F(s)$
Multiplication by a constant	$Kf(t)$	$KF(s)$
Addition/subtraction	$f_1(t) + f_2(t) - f_3(t) + \dots$	$F_1(s) + F_2(s) - F_3(s) + \dots$
First derivative (time)	$\frac{df(t)}{dt}$	$sF(s) - f(0^-)$
Second derivative (time)	$\frac{d^2f(t)}{dt^2}$	$s^2F(s) - sf(0^-) - \frac{df(0^-)}{dt}$
$n$ th derivative (time)	$\frac{d^n f(t)}{dt^n}$	$s^n F(s) - s^{n-1}f(0^-) - s^{n-2} \frac{df(0^-)}{dt} - s^{n-3} \frac{d^2f(0^-)}{dt^2} - \dots - \frac{d^{n-1}f(0^-)}{dt^{n-1}}$
Time integral	$\int_0^t f(x) dx$	$\frac{F(s)}{s}$
Translation in time	$f(t - a)u(t - a)$ , $a > 0$	$e^{-as}F(s)$
Translation in frequency	$e^{-at}f(t)$	$F(s + a)$
Scale changing	$f(at)$ , $a > 0$	$\frac{1}{a}F\left(\frac{s}{a}\right)$
First derivative ( $s$ )	$tf(t)$	$-\frac{dF(s)}{ds}$
$n$ th derivative ( $s$ )	$t^n f(t)$	$(-1)^n \frac{d^n F(s)}{ds^n}$
$s$ integral	$\frac{f(t)}{t}$	$\int_s^\infty F(u) du$

TABLE 12.3 Four Useful Transform Pairs

Pair Number	Nature of Roots	$F(s)$	$f(t)$
1	Distinct real	$\frac{K}{s + a}$	$Ke^{-at}u(t)$
2	Repeated real	$\frac{K}{(s + a)^2}$	$Kte^{-at}u(t)$
3	Distinct complex	$\frac{K}{s + \alpha - j\beta} + \frac{K^*}{s + \alpha + j\beta}$	$2 K e^{-\alpha t} \cos(\beta t + \theta)u(t)$
4	Repeated complex	$\frac{K}{(s + \alpha - j\beta)^2} + \frac{K^*}{(s + \alpha + j\beta)^2}$	$2t K e^{-\alpha t} \cos(\beta t + \theta)u(t)$

Note: In pairs 1 and 2,  $K$  is a real quantity, whereas in pairs 3 and 4,  $K$  is the complex quantity  $|K| \angle \theta$ .

TABLE 13.1 Summary of the  $s$ -Domain Equivalent Circuits

TIME DOMAIN	FREQUENCY DOMAIN
