

Q1) For the three coupled coils in Fig. 1, calculate the total inductance

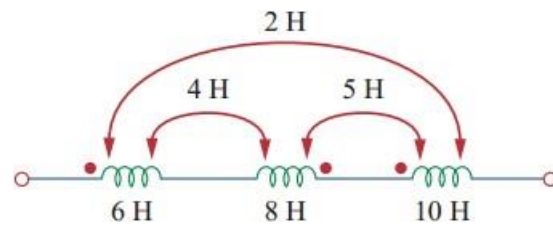


fig.1

Q2) (a) For the coupled coils in Fig. 2(a), show that $L_{eq} = L_1 + L_2 + 2M$

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

(b) For the coupled coils in Fig. 2(b), show

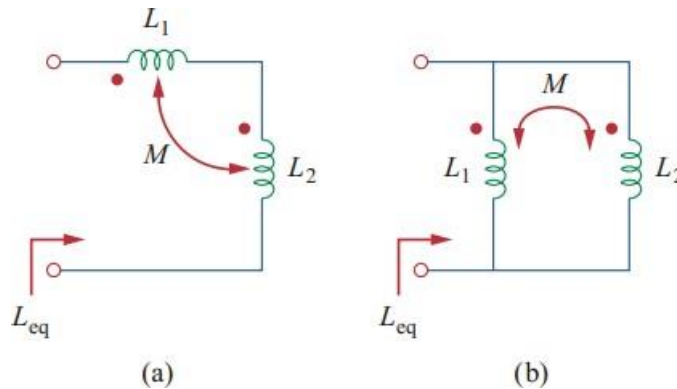


fig.2

Q3) Find current I_o in the circuit of Fig. 3

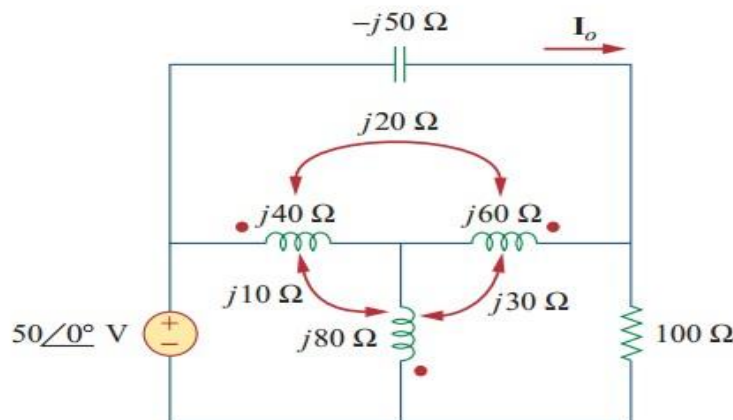


fig.3

Q4) If $M=0.2$ H and $V_s=120 \cos 10t$ V in the circuit of Fig. 4, find i_1 and i_2 . Calculate the energy stored in the coupled coils at $t=15$ ms

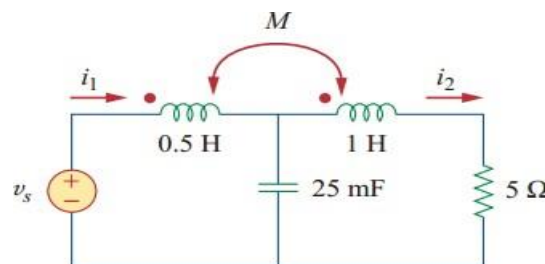


fig.4

Q5) Find currents I_1 , I_2 and I_3 in the circuit of Fig. 5

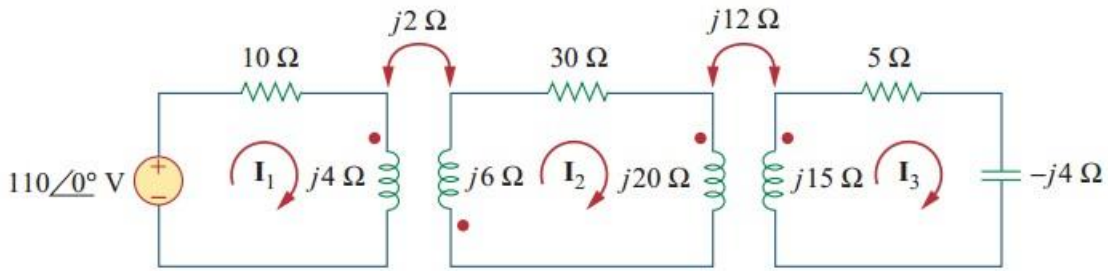


fig.5

Q6) For the circuit in Fig.6, find I_1 , I_2 , and V_o


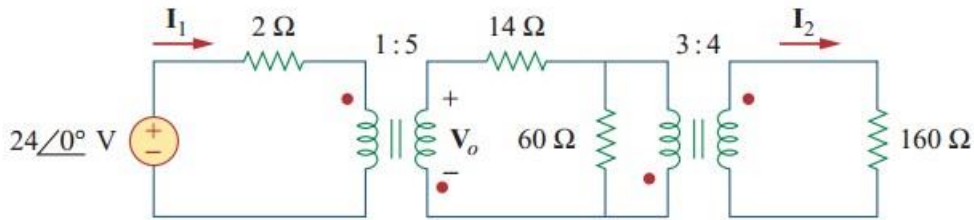


fig.6

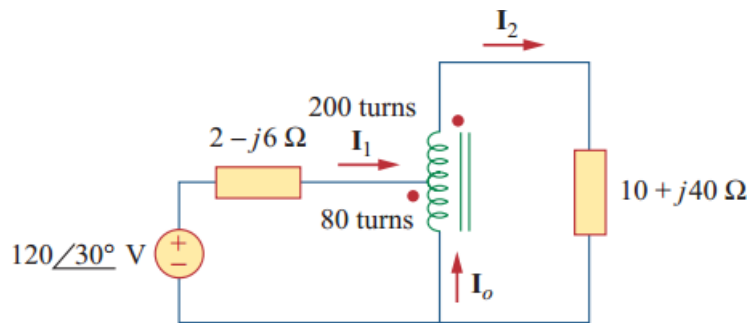Q7) In the ideal autotransformer of Fig. 7, calculate I_1 , I_2 and I_o Find the average power delivered to the load



Ω⊙Ω Ω⊙Ω Ω⊙Ω Ω⊙Ω Ω⊙Ω Ω⊙Ω Ω⊙Ω Ω⊙Ω Ω⊙Ω Ω⊙Ω Ω⊙Ω