

- 1- For the circuit shown in fig.1
 - a) Determine the Q-point.
 - b) What is the maximum peak value of collector current and output voltage that can be realized?
 - c) Find the voltage gain, power gain, minimum power rating for the transistor, maximum output signal power to the load and efficiency for the amplifier.
- 2- For the circuit shown in fig.2
 - a) Determine the dc parameters $V_B(Q1)$, $V_B(Q2)$, V_E , I_{CQ} , $V_{CEQ}(Q1)$, $V_{CEQ}(Q2)$
 - b) Determine the approximate input resistance seen by the signal source for the amplifier of $\beta_{ac} = 100$.
 - c) For the 5 Vrms input, determine the power delivered to the load resistor and what is the efficiency?
- 3- For the circuit shown in fig.3
 - a) Determine the dc parameters $V_B(Q1)$, $V_B(Q2)$, V_E , I_{CQ} , $V_{CEQ}(Q1)$, $V_{CEQ}(Q2)$
 - b) Assuming the input voltage is 10 V pp, determine the power delivered to the load resistor.
 - c) What is the maximum power that could be delivered to the load resistor?
- 4- A certain class C amplifier transistor is on for 10 percent of the input cycle if $V_{ce(sat)} = 0.18 \text{ V}$, $I_{c(sat)} = 25 \text{ mA}$, $V_{CC} = 15 \text{ V}$ and the equivalent parallel resistance in the collector tank circuit is 50Ω .
 - a) what is the average power dissipation for maximum output?
 - b) What is the maximum peak-to-peak output voltage and Determine the efficiency
 - c) What is the resonant frequency of a tank circuit with $L = 10 \text{ mH}$ and $C = 0.001 \mu\text{F}$

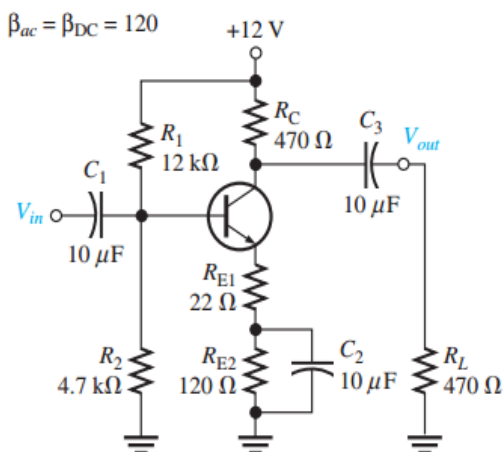


Figure 1

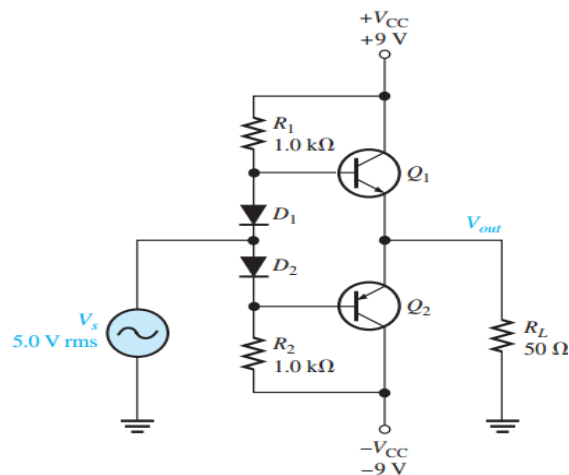


Figure 2

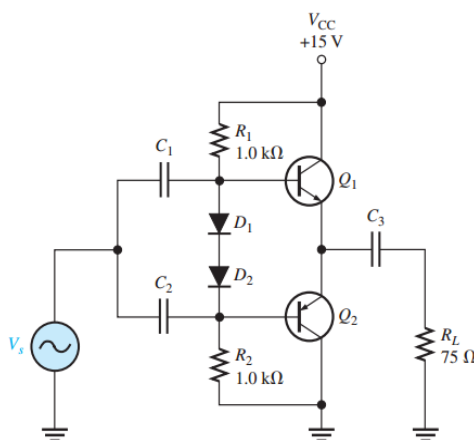


Figure 3