

1- For the circuit shown in fig.1&2

- Determine the critical frequencies associated with the low-frequency response of the amplifier.
- Determine the critical frequencies associated with the high-frequency response of the amplifier.
- Which is the dominant critical frequency and Sketch the Bode plot.
- Determine the voltage gain of the amplifier at one-tenth of the dominant critical frequency, at the dominant critical frequency, and at ten times the dominant critical frequency for the low-frequency response.
- Determine the phase shift at each of the frequencies used in d.
- What is the bandwidth of the amplifier.

2- For the circuit shown in fig.3

- Determine the lower critical frequencies. Assume that the load is another identical amplifier with the same R_{in} . The datasheet shows I_{GSS} 100 nA at $V_{GS}=-12$ V.
- Find the upper critical frequency for the FET amplifier where $C_{iss}=8$ pF, $C_{rss}=3$ pF, and $g_m=6500$ mS

- In a certain two-stage amplifier**, the lower critical frequencies are $f_{cl(1)}=125$ Hz and $f_{cl(2)}= 125$ Hz, and the upper critical frequencies are $f_{cu(1)}=3$ MHz and $f_{cu(2)}=2.5$ MHz Determine the bandwidth.
- What is the dominant lower critical frequency of a three-stage amplifier in which $f_{cl}=50$ Hz for each stage.
- $f_T=200$ MHz is taken from the datasheet of a transistor used in a certain amplifier. If the midrange gain is determined to be 38 and if f_{cl} is low enough to be neglected compared to f_{cu} , what bandwidth would you expect? What value of f_{cu} would you expect?

Assignment Design CE amplifier has a voltage gain of 100 and bandwidth of 1 MHz, maximum power consumption accepted is 50 mW from 12 V DC supply.

 


Figure 1

 


Figure 2

 


Figure 3