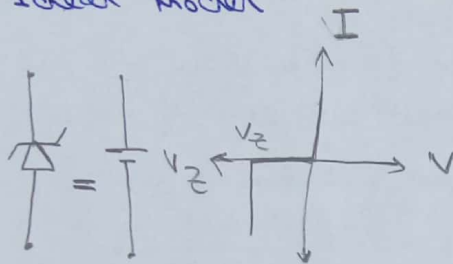


⇒ The Zener Diode


The Zener is a silicon PN junction that is designed to operate in the reverse breakdown region. When the Zener reaches reverse breakdown, its voltage remains constant even though the current changes drastically.

⊗ Zener equivalent Circuits

1) Ideal Model



2) Practical Model

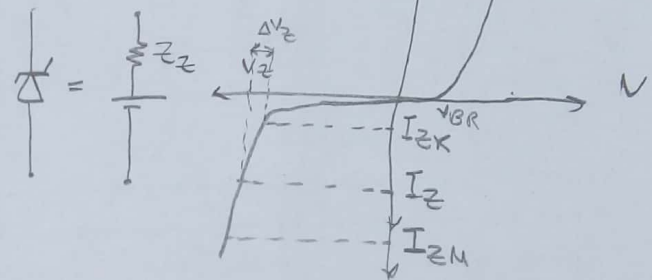

$$\rightarrow Z_Z = \frac{\Delta V_Z}{\Delta I_Z}$$

→ I_{ZK} is the minimum reverse current required to keep the Zener in breakdown for voltage regulation

→ I_{ZM} is the maximum reverse current above it the Zener may be damaged.

note that $I_{ZK} < I_Z < I_{ZM}$ to keep the reverse voltage across the Zener constant.

→ The Zener voltage change with the change in temperature according to

$$\Delta V_Z = V_Z * TC * \Delta T$$

$$\Delta V_Z = TC * \Delta T$$

$$I_{ZM} = \frac{P_{D(max)}}{V_Z}$$

where TC is Percentage

where TC is in mV

⊗ Zener Diode Application

- 1- Zener regulation with a variable input voltage.
- 2- Zener regulation with variable load.
- 3- Zener limiter

$$\text{Line regulation} = \frac{\Delta V_{out}}{\Delta V_{in}}$$

$$\text{Load regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}}$$

□

Sheet # 5

1] given $Z_z = 15 \Omega$, $V_{z_1} = 4.7 \text{ V}$ at $I_{z_1} = 25 \text{ mA}$
 find V_{z_2} at $I_{z_2} = 50 \text{ mA}$.

→
$$Z_z = \frac{\Delta V_z}{\Delta I_z} = \frac{V_{z_2} - 4.7}{(50 - 25) \times 10^{-3}} = 15 \Rightarrow V_{z_2} = 5.075 \text{ V}$$

2] given $V_z = 6.8 \text{ V}$ at 25°C and $TC = +0.004\%/^\circ \text{C}$
 find V_z at 70°C


→
$$\Delta V_z = V_z \times TC \times \Delta T = 6.8 \times (0.004/100) \times (70 - 25) = 12 \text{ mV}$$

 then the Zener voltage at $70^\circ \text{C} = V_z + \Delta V_z = 6.8 + 0.012 = 6.812 \text{ V}$


3] given $I_{zK} = 1.5 \text{ mA}$ and $V_z = 14 \text{ V}$

→
$$V_{in(\text{min})} = V_R + V_z = I_{zK} \times R + V_z$$
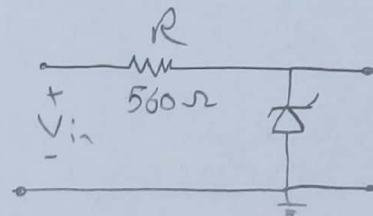
$$V_{in(\text{min})} = 1.5 \times 0.56 + 14 = 14.84 \text{ V}$$



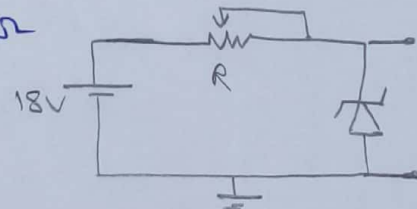4] given $V_z = 12 \text{ V}$ at $I_z = 30 \text{ mA}$ and $Z_z = 30 \Omega$
 find R for $I_z = 40 \text{ mA}$





→
$$\Delta V_z = \Delta I_z Z_z = (40 - 30) \times 10^{-3} \times 30 = 0.3 \text{ V}$$

 then V_z at $I_z = 40 \text{ mA} = V_z + \Delta V_z = 12 + 0.3 = 12.3 \text{ V}$

$$V_R = V_{in} - V_z = 18 - 12.3 = 5.7 \text{ V}$$

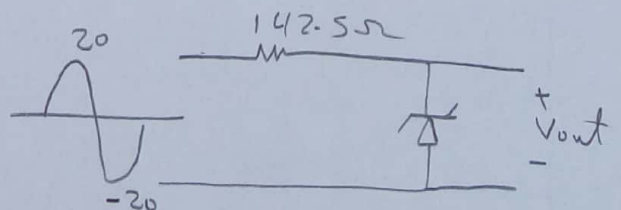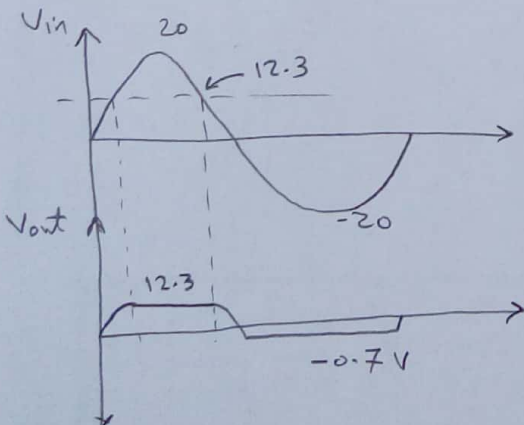 then $R = 5.7 / 40 \text{ mA} = 142.5 \Omega$



2]

5) given $V_Z = 5.1 \text{ V}$ at $I_Z = 49 \text{ mA}$, $I_{ZK} = 1 \text{ mA}$, $I_{ZM} = 70 \text{ mA}$ and $Z_Z = 7 \Omega$
 find $I_{L(\min)}$, $I_{L(\max)}$



⊗ Maximum Load Current

$$V_Z(\min) = V_Z - \Delta I_Z Z_Z$$

$$V_Z(\min) = 5.1 - (49 - 1) \times 10^{-3} \times 7 = 4.764 \text{ V}$$

$$I_T = [V_{in} - V_Z(\min)] / R = (8 - 4.764) / 22 = 147 \text{ mA}$$


$$I_{L(\max)} = I_T - I_{ZK} = 146 \text{ mA}$$

⊗ Minimum Load Current

$$V_Z(\max) = V_Z + \Delta I_Z Z_Z = 5.1 + (70 - 49) \times 10^{-3} \times 7 = 5.247 \text{ V}$$

$$I_T = (V_{in} - V_Z) / R = 125.1 \text{ mA}$$
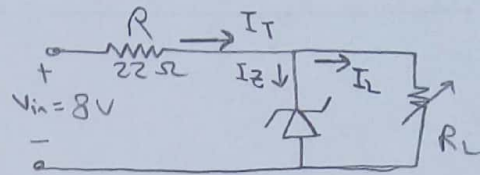
$$I_{Z(\min)} = I_T - I_{ZM} = 55.1 \text{ mA}$$



⊗ Example: Determine the output voltage waveform for each circuit

