

Sheet 2

Problem1

A lossless transmission line of electrical length $l = 0.35\lambda$ is terminated in a load impedance as shown in Fig. P4. Find Γ_L , SWR, Γ_{in} and Z_{in} .

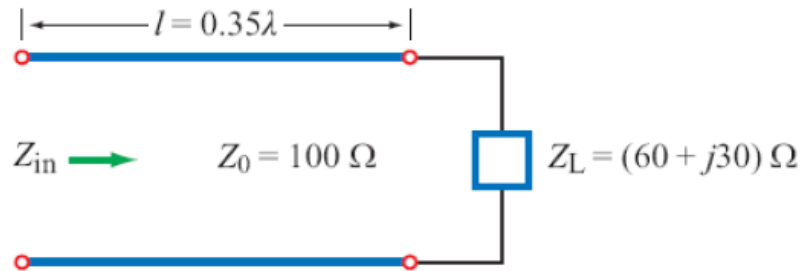


Fig. P4: Circuit for Problem P4.

Problem2

Two half-wave dipole antennas, each with an impedance of 75Ω , are connected in parallel through a pair of transmission lines, and the combination is connected to a feed transmission line, as shown in Fig. P5.

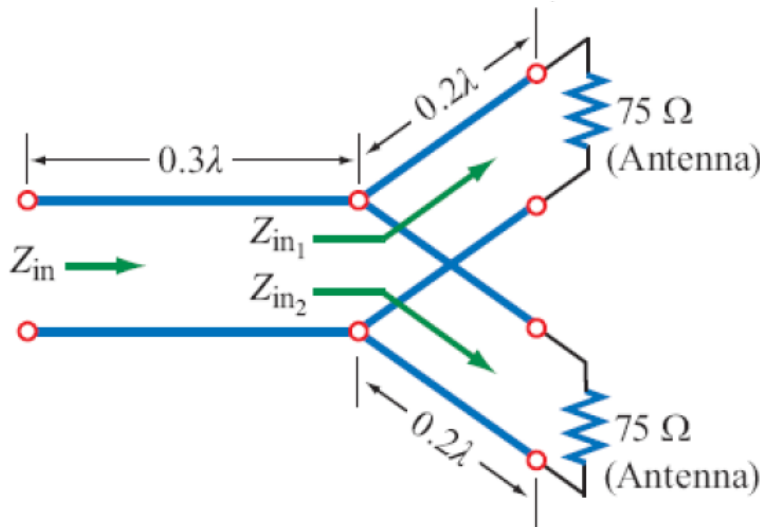


Fig. P5: Circuit for Problem P5.

All lines are 50Ω and lossless.

- Calculate Z_{in1} , the input impedance of the antenna-terminated line, at the parallel juncture.
- Combine Z_{in1} and Z_{in2} in parallel to obtain Z'_L , the effective load impedance of the feedline.
- Calculate Z_{in} of the feedline.

Problem3

- 2.11 A $100\ \Omega$ transmission line has an effective dielectric constant of 1.65. Find the shortest open-circuited length of this line that appears at its input as a capacitor of 5 pF at 2.5 GHz. Repeat for an inductance of 5 nH.

Problem4

- 2.17 For a purely reactive load impedance of the form $Z_L = jX$, show that the reflection coefficient magnitude $|\Gamma|$ is always unity. Assume that the characteristic impedance Z_0 is real.

Problem5


- 2.12 A lossless transmission line is terminated with a $100\ \Omega$ load. If the SWR on the line is 1.5, find the two possible values for the characteristic impedance of the line.

Problem6

] The results of a slotted-line experiment are plotted in the following figure.


The length of the line is $\ell = 8.4\text{ cm}$; its characteristic impedance is $Z_0 = 50\ \Omega$. Find

- (a) The reflection coefficient at the load.
- (b) The load impedance.
- (c) The input impedance.
- (d) The reflection coefficient at the generator terminals.

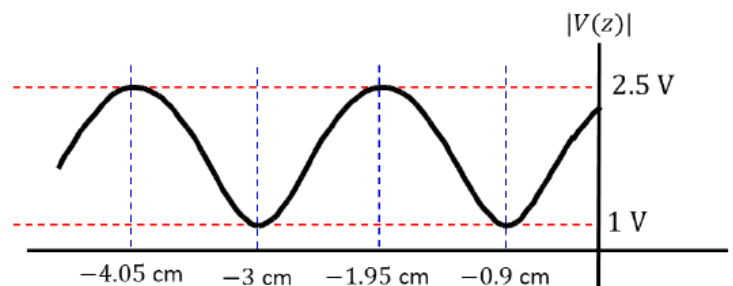

Problem7

- 2.19 A generator is connected to a transmission line as shown in the accompanying figure. Find the voltage as a function of z along the transmission line. Plot the magnitude of this voltage for $-\ell \leq z \leq 0$.

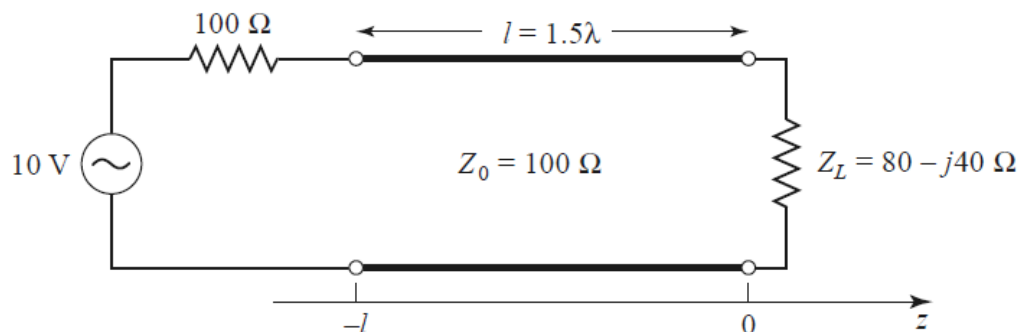

Problem8

- 2.14 A radio transmitter is connected to an antenna having an impedance $80 + j40\ \Omega$ with a $50\ \Omega$ coaxial cable. If the $50\ \Omega$ transmitter can deliver 30 W when connected to a $50\ \Omega$ load, how much power is delivered to the antenna?

Problem9

2.16 The transmission line circuit in the accompanying figure has $V_g = 15$ V rms, $Z_g = 75 \Omega$, $Z_0 = 75 \Omega$, $Z_L = 60 - j40 \Omega$, and $\ell = 0.7\lambda$. Compute the power delivered to the load using three different techniques:

(a) Find Γ and compute

$$P_L = \left(\frac{V_g}{2} \right)^2 \frac{1}{Z_0} (1 - |\Gamma|^2);$$

(b) find Z_{in} and compute

$$P_L = \left| \frac{V_g}{Z_g + Z_{in}} \right|^2 \operatorname{Re} \{Z_{in}\};$$

(c) find V_L and compute

$$P_L = \left| \frac{V_L}{Z_L} \right|^2 \operatorname{Re} \{Z_L\}.$$

Discuss the rationale for each of these methods. Which of these methods can be used if the line is not lossless?

Problem10

2.29 A 50Ω transmission line is matched to a 10 V source and feeds a load $Z_L = 100 \Omega$. If the line is 2.3λ long and has an attenuation constant $\alpha = 0.5$ dB/ λ , find the powers that are delivered by the source, lost in the line, and delivered to the load.