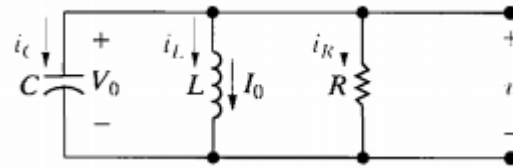



Q1: The natural voltage response of the circuit in Fig.Q1 is

$$v(t) = 75e^{-8000t}(\cos 6000t - 4 \sin 6000t)V, \quad t \geq 0,$$




When the inductor is 400mH. Find (a)C; (b)R; (c)V<sub>0</sub>; (d)I<sub>0</sub>; and (e)I<sub>L(t)</sub>.

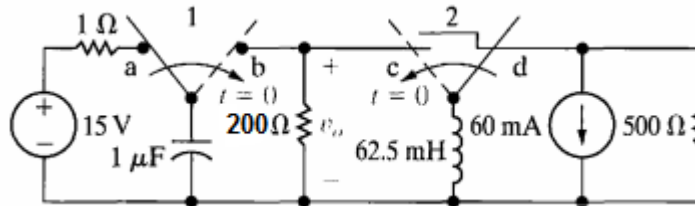Q2: The two switches in the circuit seen in Fig.Q2 operate synchronously. When switch 1 is in position a, switch 2 is in position d. When switch 1 moves to position b, switch 2 moves to position c. Switch 1 has been in position a for a long time. At t=0, the switches move to their alternate positions. Find v<sub>o(t)</sub> for t>0.




Q3: The resistor in the circuit of Fig.Q2 is decreased from 200 Ω to 125 Ω. Find v<sub>o(t)</sub> for t>0.

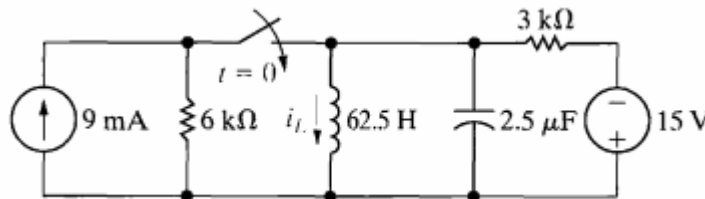Q4: The switch in the circuit in Fig. Q4 has been Open a long time before closing at t=0 find i<sub>l(t)</sub> for t≥0.




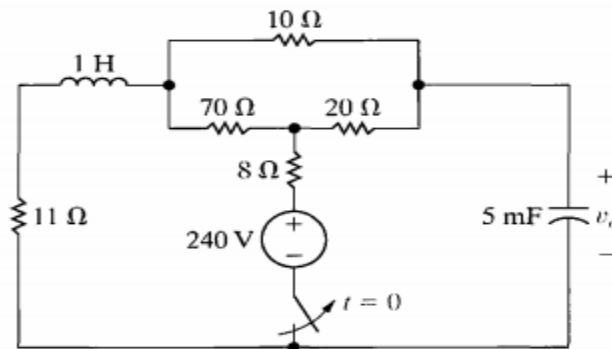Q5: The switch in the circuit shown in Fig.Q5 has been closed for a long time. The switch opens at t=0. Find v<sub>o(t)</sub> for t>0.



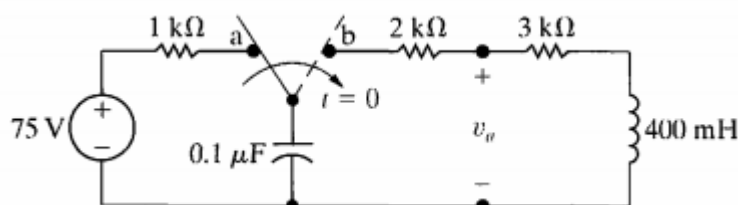
Q6: The switch in the circuit in Fig.Q6 has been in position a for a long time. At t=0, the switch moves instantaneously to position b.

- What is the initial value of v<sub>a</sub>?
- What is the initial value of dv<sub>a</sub>/dt?
- What is the numerical expression for v<sub>a(t)</sub> for t>0?



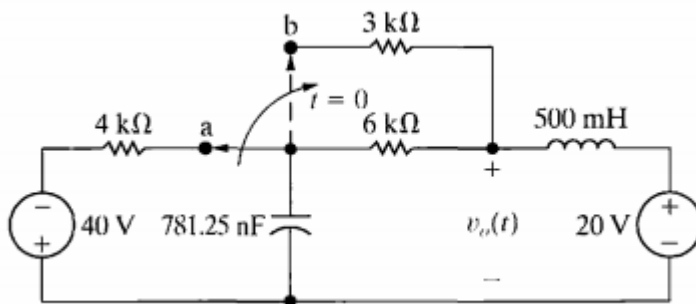Q7: The switch in the circuit of Fig.Q7 has been in position a for a long time. At  $t=0$  the switch moves instantaneously to position b. Find


- $v_o(0^+)$
- $dv_o(0^+)/dt$
- $v_o(t)$  for  $t \geq 0$ .



Q8: a) Derive the differential equation that relates The output voltage to the input voltage for the circuit shown in Fig.Q8.


b) Compare the result with Eq.8.75 when  $R_1C_1=R_2C_2=RC$  in Fig.8.18.

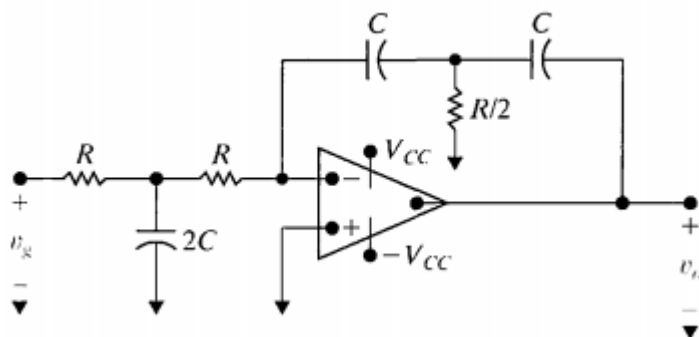c) What is the advantage of the circuit shown in Fig.Q8?




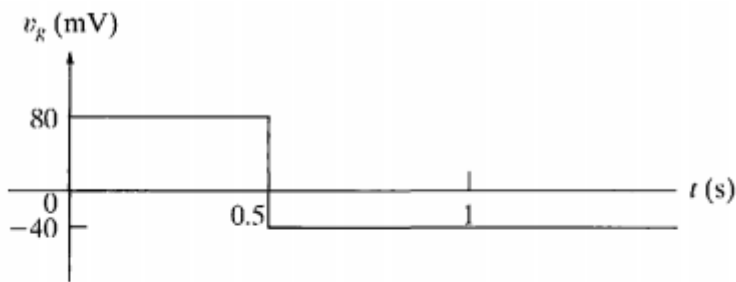Q9: The voltage signal of Fig.Q9 (a) is applied to cascaded integrating amplifiers shown in Fig.Q9(b). There is no energy stored in the capacitors at the instant the signal is applied.

- Derive the numerical expressions for  $v_o(t)$  and  $v_{o1}(t)$  for the time intervals  $0 < t < 0.5$  s and  $0.5$  s  $< t < t_{sat}$ .
- Compute the value of  $t_{sat}$ .



(a)

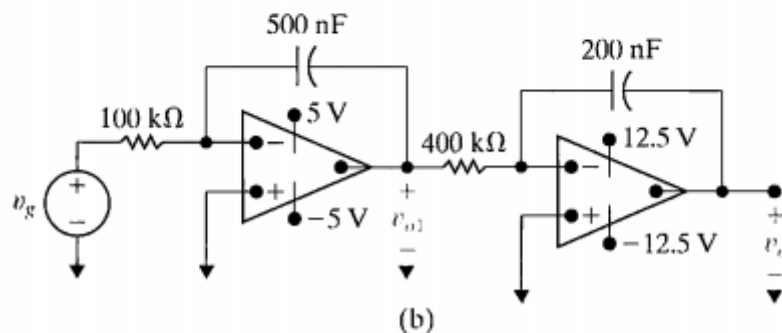

(b)